

Name: Solutions

For the circuit shown below find the transfer function $\frac{V_R(s)}{V(s)}$ in terms of R , L , and C .

$$V(t) = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$


LT

$$V(s) = R I(s) + L s I(s) + \frac{1}{C} \frac{I(s)}{s}$$

$$V_R(t) = R i(t)$$

LT

$$V_R(s) = R I(s)$$

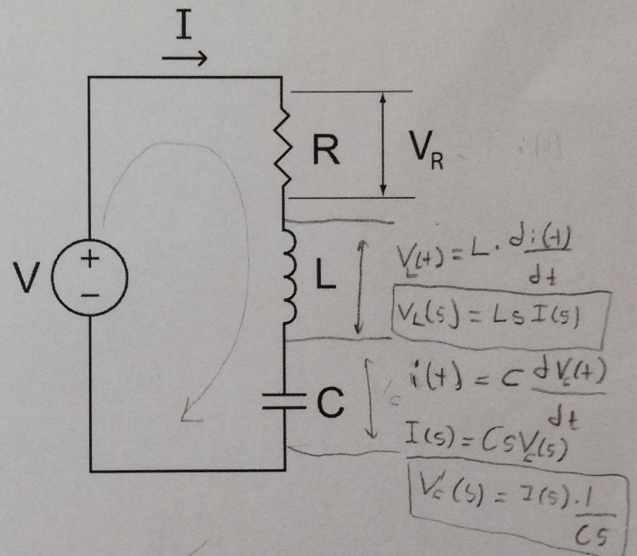

$$\frac{V_R(s)}{V(s)} = \frac{R \cdot I(s)}{R I(s) + L \cdot s \cdot I(s) + \frac{1}{C} \frac{I(s)}{s}} = \frac{R \cdot I(s)}{I(s) \left(R + sL + \frac{1}{Cs} \right)} = \frac{R}{R + sL + \frac{1}{Cs}}$$